

UC200A-GL

Reference Design

UMTS/HSPA+ Module Series

Version: 1.0

Date: 2023-03-03

Status: Released



At Quectel, our aim is to provide timely and comprehensive services to our customers. If you require any assistance, please contact our headquarters:

Quectel Wireless Solutions Co., Ltd.

Building 5, Shanghai Business Park Phase III (Area B), No.1016 Tianlin Road, Minhang District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: info@quectel.com

Or our local offices. For more information, please visit:

<http://www.quectel.com/support/sales.htm>.

For technical support, or to report documentation errors, please visit:

<http://www.quectel.com/support/technical.htm>.

Or email us at: support@quectel.com.

Legal Notices

We offer information as a service to you. The provided information is based on your requirements and we make every effort to ensure its quality. You agree that you are responsible for using independent analysis and evaluation in designing intended products, and we provide reference designs for illustrative purposes only. Before using any hardware, software or service guided by this document, please read this notice carefully. Even though we employ commercially reasonable efforts to provide the best possible experience, you hereby acknowledge and agree that this document and related services hereunder are provided to you on an “as available” basis. We may revise or restate this document from time to time at our sole discretion without any prior notice to you.

Use and Disclosure Restrictions

License Agreements

Documents and information provided by us shall be kept confidential, unless specific permission is granted. They shall not be accessed or used for any purpose except as expressly provided herein.

Copyright

Our and third-party products hereunder may contain copyrighted material. Such copyrighted material shall not be copied, reproduced, distributed, merged, published, translated, or modified without prior written consent. We and the third party have exclusive rights over copyrighted material. No license shall be granted or conveyed under any patents, copyrights, trademarks, or service mark rights. To avoid ambiguities, purchasing in any form cannot be deemed as granting a license other than the normal non-exclusive, royalty-free license to use the material. We reserve the right to take legal action for noncompliance with abovementioned requirements, unauthorized use, or other illegal or malicious use of the material.

Trademarks

Except as otherwise set forth herein, nothing in this document shall be construed as conferring any rights to use any trademark, trade name or name, abbreviation, or counterfeit product thereof owned by Quectel or any third party in advertising, publicity, or other aspects.

Third-Party Rights

This document may refer to hardware, software and/or documentation owned by one or more third parties (“third-party materials”). Use of such third-party materials shall be governed by all restrictions and obligations applicable thereto.

We make no warranty or representation, either express or implied, regarding the third-party materials, including but not limited to any implied or statutory, warranties of merchantability or fitness for a particular purpose, quiet enjoyment, system integration, information accuracy, and non-infringement of any third-party intellectual property rights with regard to the licensed technology or use thereof. Nothing herein constitutes a representation or warranty by us to either develop, enhance, modify, distribute, market, sell, offer for sale, or otherwise maintain production of any our products or any other hardware, software, device, tool, information, or product. We moreover disclaim any and all warranties arising from the course of dealing or usage of trade.

Privacy Policy

To implement module functionality, certain device data are uploaded to Quectel’s or third-party’s servers, including carriers, chipset suppliers or customer-designated servers. Quectel, strictly abiding by the relevant laws and regulations, shall retain, use, disclose or otherwise process relevant data for the purpose of performing the service only or as permitted by applicable laws. Before data interaction with third parties, please be informed of their privacy and data security policy.

Disclaimer

- a) We acknowledge no liability for any injury or damage arising from the reliance upon the information.
- b) We shall bear no liability resulting from any inaccuracies or omissions, or from the use of the information contained herein.
- c) While we have made every effort to ensure that the functions and features under development are free from errors, it is possible that they could contain errors, inaccuracies, and omissions. Unless otherwise provided by valid agreement, we make no warranties of any kind, either implied or express, and exclude all liability for any loss or damage suffered in connection with the use of features and functions under development, to the maximum extent permitted by law, regardless of whether such loss or damage may have been foreseeable.
- d) We are not responsible for the accessibility, safety, accuracy, availability, legality, or completeness of information, advertising, commercial offers, products, services, and materials on third-party websites and third-party resources.

Copyright © Quectel Wireless Solutions Co., Ltd. 2023. All rights reserved.

About the Document

Revision History

Version	Date	Author	Description
-	2022-10-19	Coco CHEN	Creation of the document
1.0	2023-03-03	Coco CHEN	First official release

Contents

About the Document.....	3
Contents.....	4
1 Reference Design.....	5
1.1. Introduction.....	5
1.2. Schematics.....	5

1 Reference Design


1.1. Introduction

This document provides the reference design for Quectel UC200A-GL module, including the design of power supply, module interfaces, (U)SIM interface, SD card interfaces and audio interfaces, etc.

1.2. Schematics

The schematics illustrated in the following pages are provided for your reference only.

Block Diagram

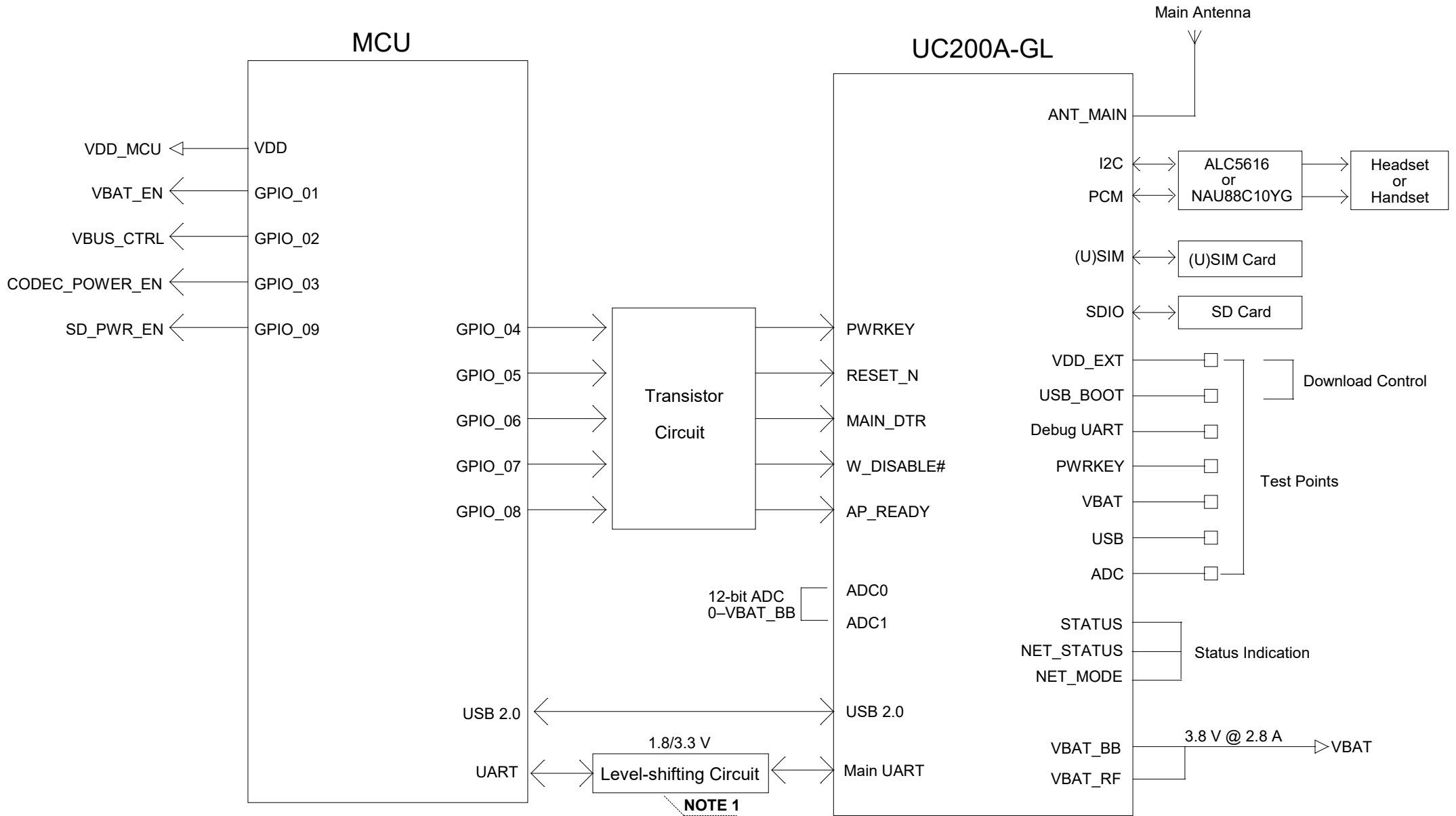


NOTE:


1. A level-shifting circuit or a voltage-level translator TXS0108EPWR provided by Texas Instruments is recommended.
2. The power supply should be able to provide sufficient current up to 2.8 A for the module.

Quectel Wireless Solutions	
PROJECT UC200A-GL	VER 1.0
DRAWN BY Cico CHEN	CHECKED BY Shiyu ZHU
DATE Feb 09, March 08, 2022	SIZE A2
1 SHEET	1 OF 13








Power System Block Diagram

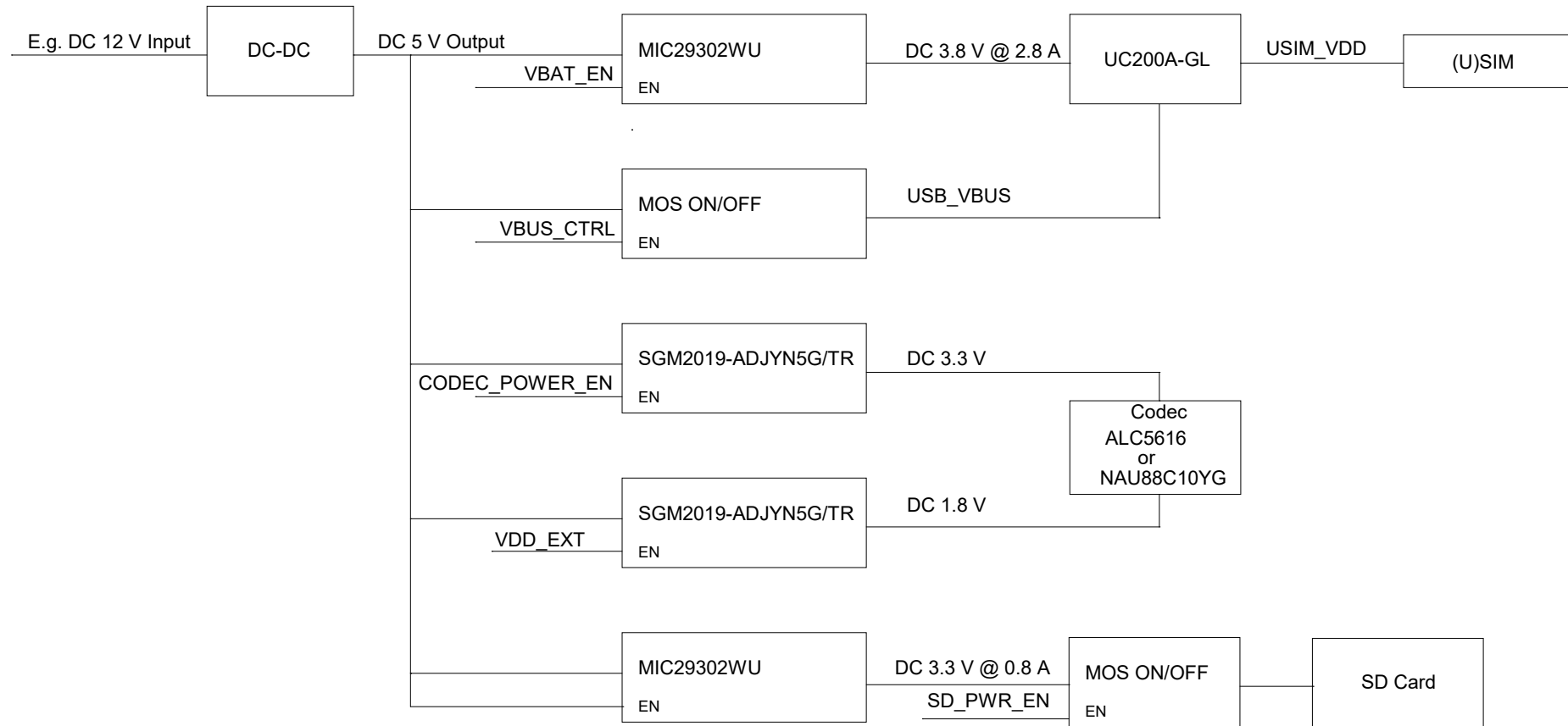

Module Interfaces

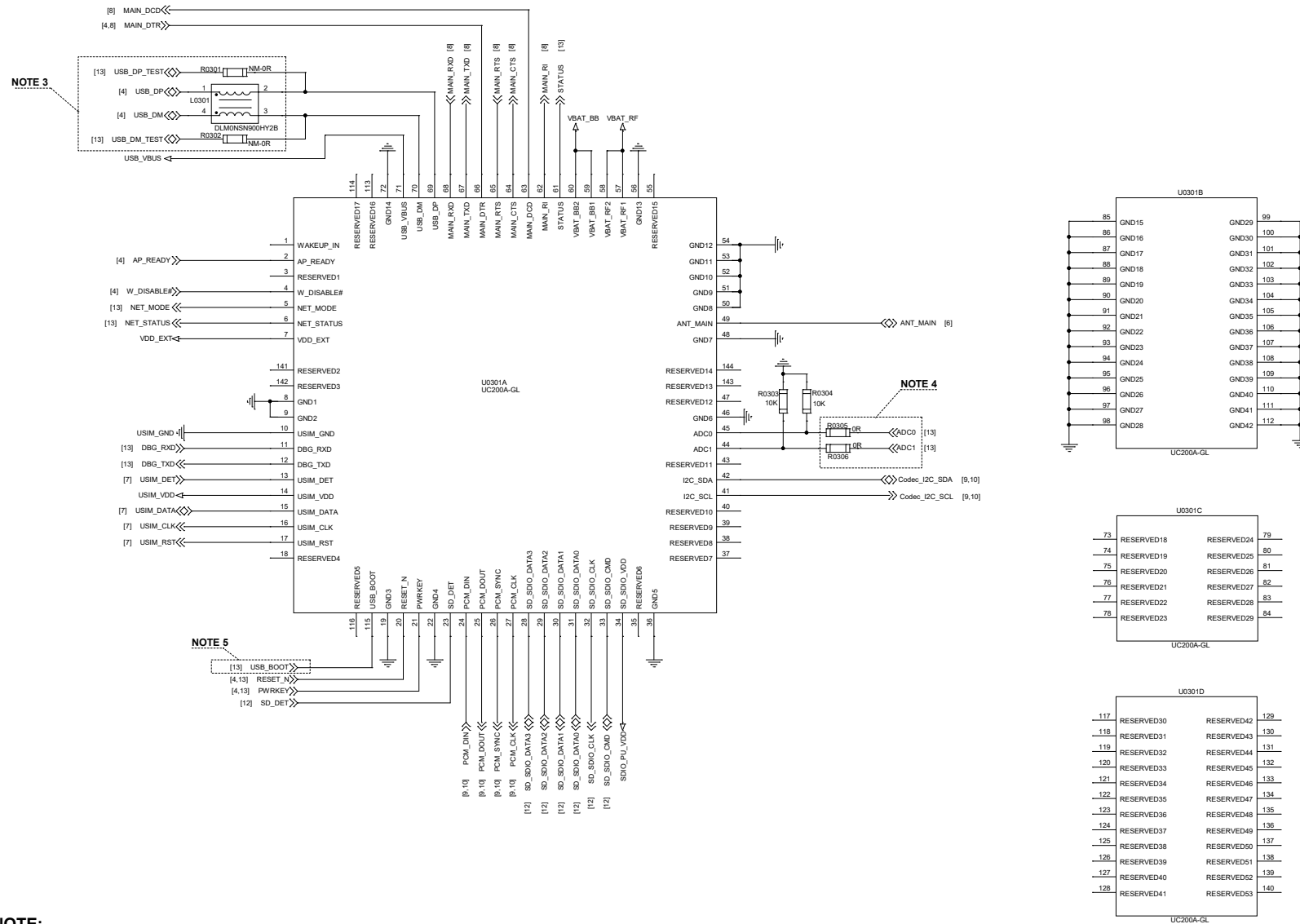

MCU Interfaces

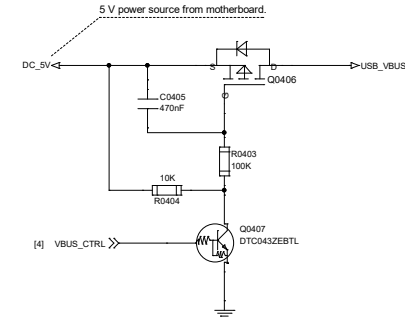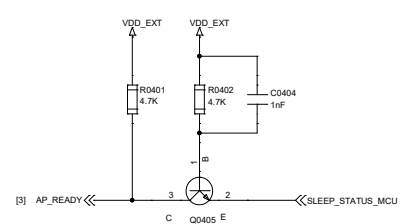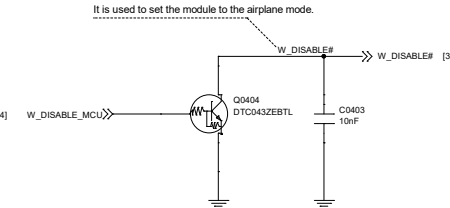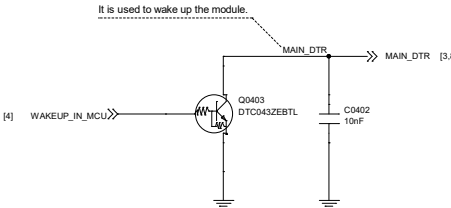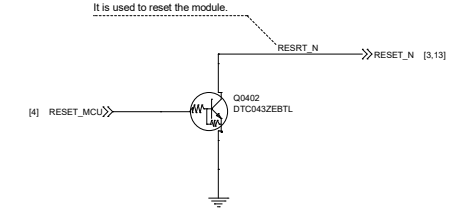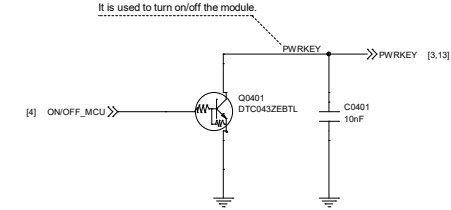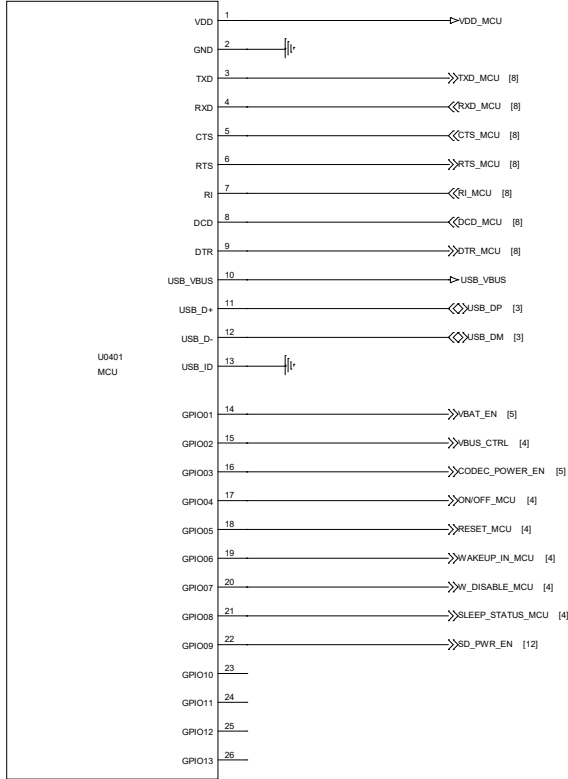


NOTE:

- U0401 represents your MCU. The power domain of GPIO interfaces of the module is 1.8 V. If the GPIO interfaces of U0401 is also 1.8 V, then the related level-shifting circuit is not needed.
- The USB interface of the module only serves as a slave device and supports full-speed and high-speed modes of USB 2.0. To communicate with the USB interface, MCU needs to support USB host mode or OTG function.
The USB_VBUS pin of the module should be powered by an external power system for USB detection, and VBUS_CTRL is used to turn on/off the USB_VBUS power supply.
- It is recommended to select GPIO pins which are at low level by default as the control pins for PWRKEY and RESET_N of the module.
Ensure that the maximum load capacitance does not exceed 10 nF on PWRKEY and RESET_N pins.

Power Supply Design


DC-DC Application

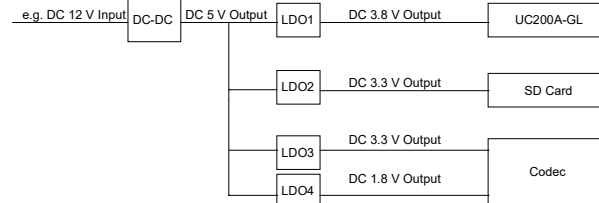When the input voltage is above 7.0 V, use a DC-DC converter to convert a high input voltage into a 5.0 V output, and then use LDOs to convert it to 3.8 V, 3.3 V and 1.8 V voltages to power the module, SD card and codec.




LDO Application

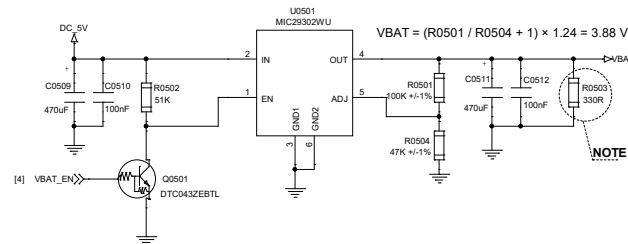When the input voltage is below 7.0 V, use a LDO to convert it to 3.8 V.




NOTE:
The recommended load current is greater than 10 mA.

Power Supply for SD Card

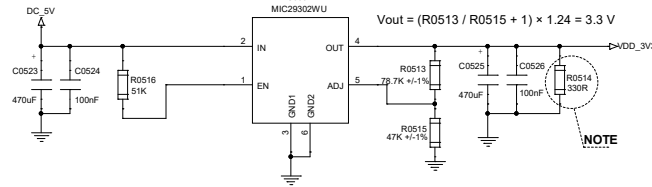

NOTE:
The recommended load current is greater than 10 mA.



VBAT Design

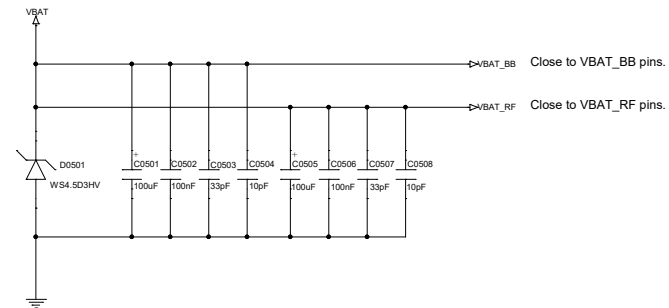

NOTE:

1. The power supply should be able to provide sufficient current up to 2.8 A for the module.
2. VBAT should be routed in star configuration to VBAT_BB and VBAT_RF pins.
3. The width of VBAT_BB trace should be not less than 1 mm and the width of VBAT_RF trace should be not less than 2 mm.
4. The recommended operating voltage of VBAT is 3.4–4.5 V and the typical value is 3.8 V.

Power Supply for Codec

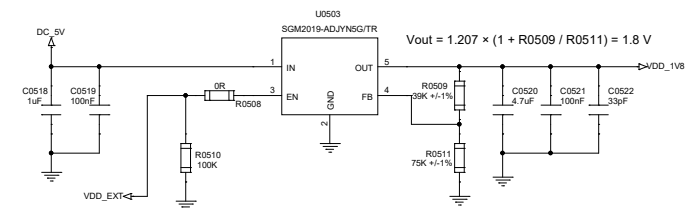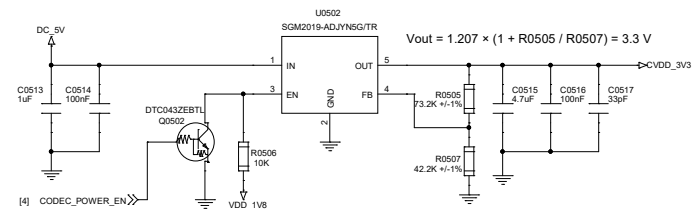


NOTE:

1. VDD_EXT and CODEC_POWER_EN are used to turn on/off VDD_1V8 and VDD_3V3 respectively.
2. The following power-up/down sequences should be followed to ensure the audio codec works normally.
Power-up sequence: power up VDD_1V8 first, and then VDD_3V3.
Power-down sequence: power down VDD_3V3 first, and then VDD_1V8.

Quectel Wireless Solutions

PROJECT	UC200A-GL	VER	1.0
DRAWN BY	Coco CHEN	CHECKED BY	Shiye ZHU
DATE	Friday, March 08, 2022	SHEET	5 OF 13

Antenna Interface Design

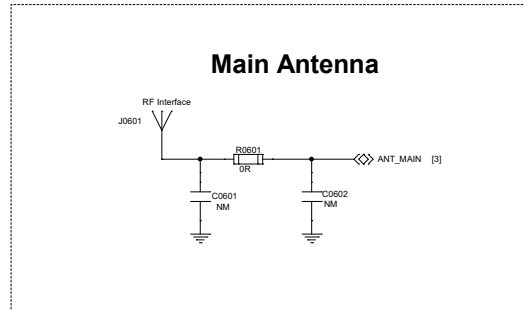


NOTE:

1. It is recommended to reserve a Π -type circuit for main antenna for future debugging.
2. The impedance of the RF signal traces must be controlled as 50 Ω when routing.

Quectel Wireless Solutions		
PROJECT	UC200A-GL	VER 1.0
DRAWN BY	Coco CHEN	CHECKED BY Shiye ZHU
DATE	F060v_Mar08.2022	SIZE A2
		SHEET 6 OF 13

(U)SIM Interface Design

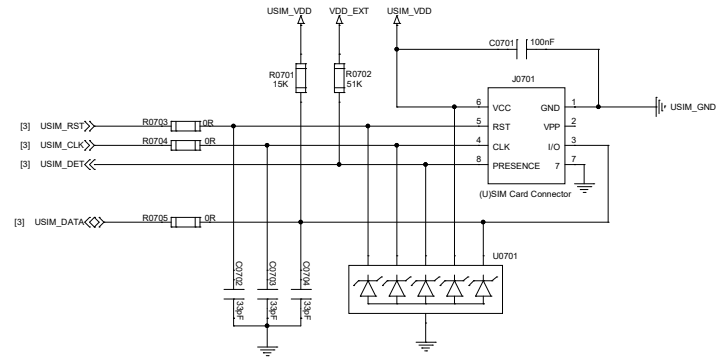

NOTE:


1. U0701 is recommended to be used to offer good ESD protection, and the parasitic capacitance should be less than 15 pF.
2. The pull-up resistor R0701 can improve anti-jamming capability, and should be placed close to the (U)SIM card connector.
3. R0703–R0705 in series between the module and (U)SIM card are used for debugging, and capacitors C0702–C0704 are used to filter out RF interference.
4. C0701 whose capacitance should be less than 1 μ F must be placed close to the (U)SIM card connector.
5. The GND of the (U)SIM card connector is recommended to be connected to the GND layer directly.
6. For more information about the layout of (U)SIM interface, see the hardware design document of the module.

Quectel Wireless Solutions


PROJECT	UC200A-GL	VER	1.0
DRAWN BY	Coco CHEN	CHECKED BY	Shiye ZHU
DATE	Friday, March 08, 2022	SIZE	A2
		SHEET	7 OF 13

UART Interface Design

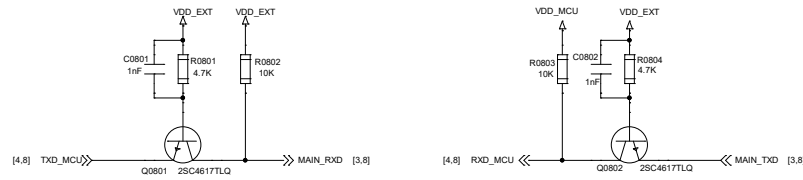UART Level-shifting Circuit - Transistor Solution



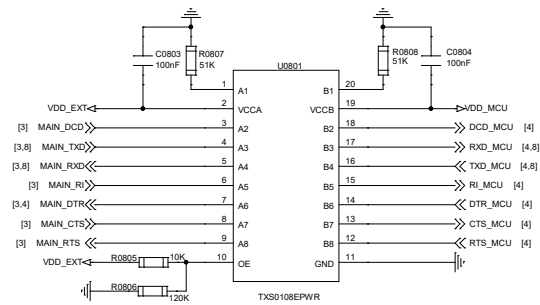UART Level-shifting Circuit - IC Solution




NOTE:

1. There are two level-shifting solutions: transistor solution and IC solution, and it is recommended to select the latter.
2. The power supply of TXS0108EPWR's VCCA should not exceed that of VCCB. For more information, see the datasheet of TXS0108EPWR.
3. The level-shifting circuit solution is not suitable for applications with high baud rates exceeding 460 kbps. The capacitors C0801 and C0802 of 1 nF can improve the signal quality.
4. MAIN_RTS and MAIN_DTR level-shifting circuits are similar to that of MAIN_RXD.
MAIN_CTS, MAIN_RI and MAIN_DCD level-shifting circuits are similar to that of MAIN_TXD.

Quectel Wireless Solutions

PROJECT	UC200A-GL	VER	1.0
DRAWN BY	Coco CHEN	CHECKED BY	Shiye ZHU
DATE	Fri, 19 March 2022	SHEET	8 OF 13

Audio Codec Design (ALC5616)


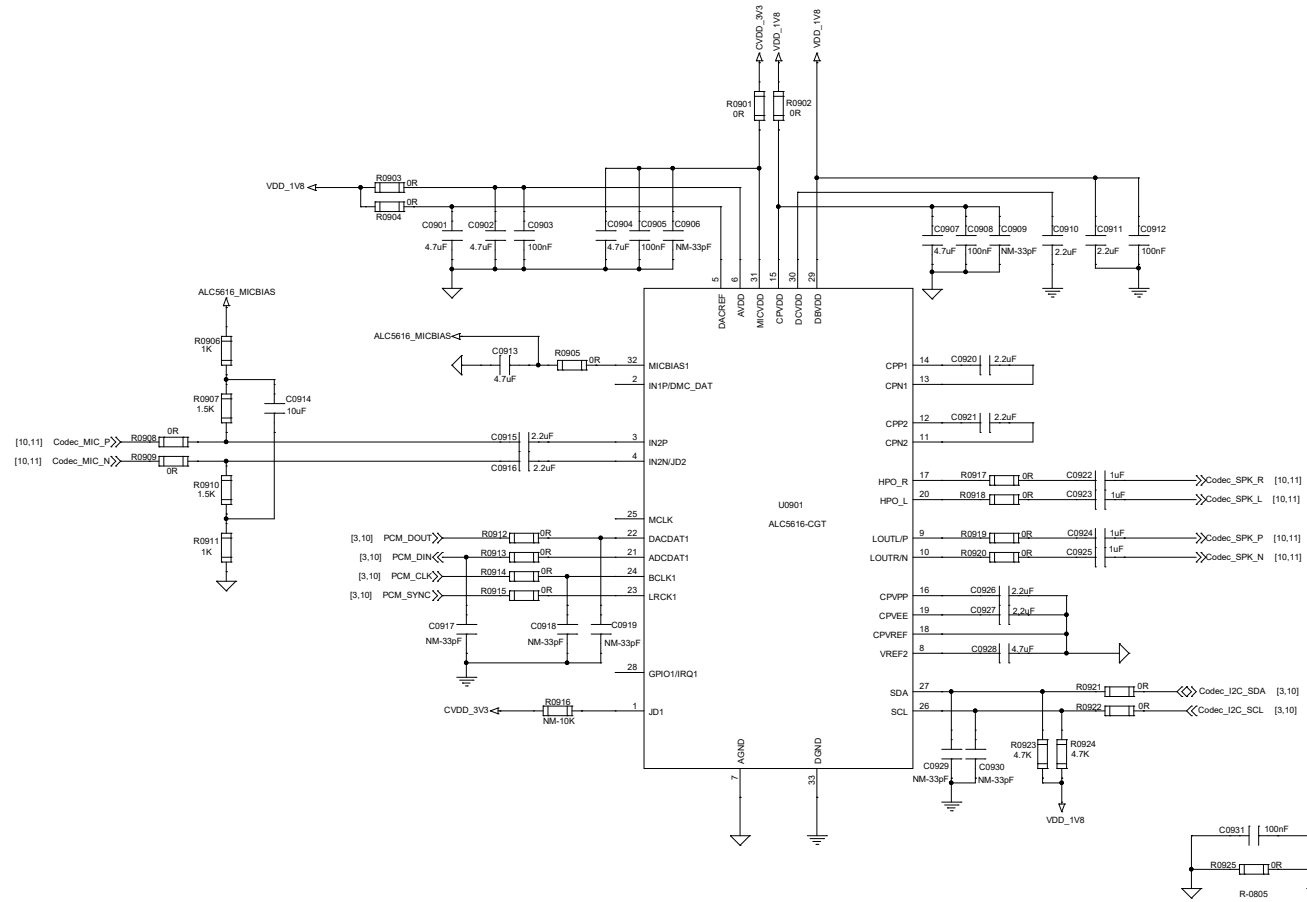


NOTE:

1. ALC5616 power-up sequence: DBVDD/I2C pull-up power/AVDD/DACREF/CPVDD → MICVDD → software initialization.
2. ALC5616 power-down sequence: disable codec function by software → MICVDD → DBVDD/I2C pull-up power/AVDD/DACREF/CPVDD.
3. The module will automatically initialize the codec via I2C interface after it is turned on successfully, so all power supplies for the codec need to be powered up before that.
4. The analog ground and digital ground need to be connected with a 0 Ω resistor packaged as R-0805. For more details, see the sheet of "Audio Codec Interface Design".
5. For more details, see the datasheet of ALC5616.

Audio Codec Design (NAU88C10YG)



Pin No.	Pin Name	Voltage	Description
2	VDDA	2.5-3.6 V	Analog VDD
4	VDDD	1.71-3.6 V	Digital VDD
17	VDDSPK	2.5-5.5 V	Loudspeaker power supply

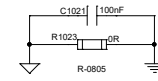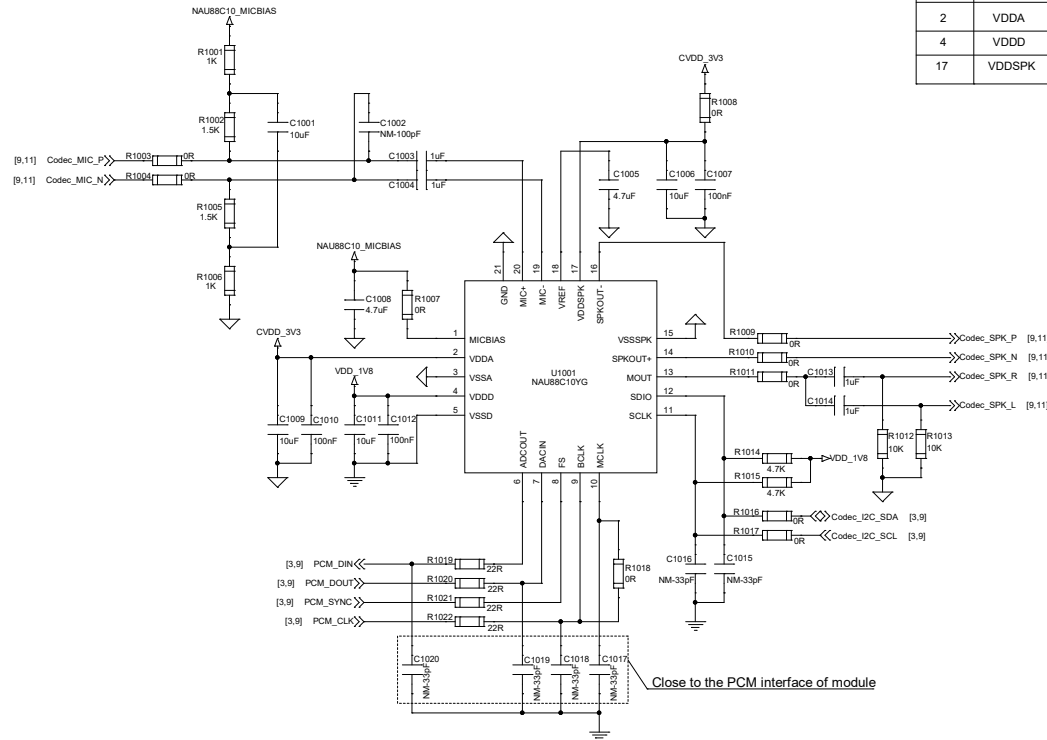

NOTE:

1. The codec should be away from interference sources such as RF and power supplies, and the codec audio signal should be surrounded with ground as much as possible.
2. The voltage of VDDA pin must always be larger than that of VDDD.
3. The analog ground and digital ground need to be connected with a 0 Ω resistor packaged as R-0805. For more details, see the sheet of "Audio Codec Interface Design."
4. For more details, see the datasheet of NAU88C10YG.

Audio Codec Interface Design

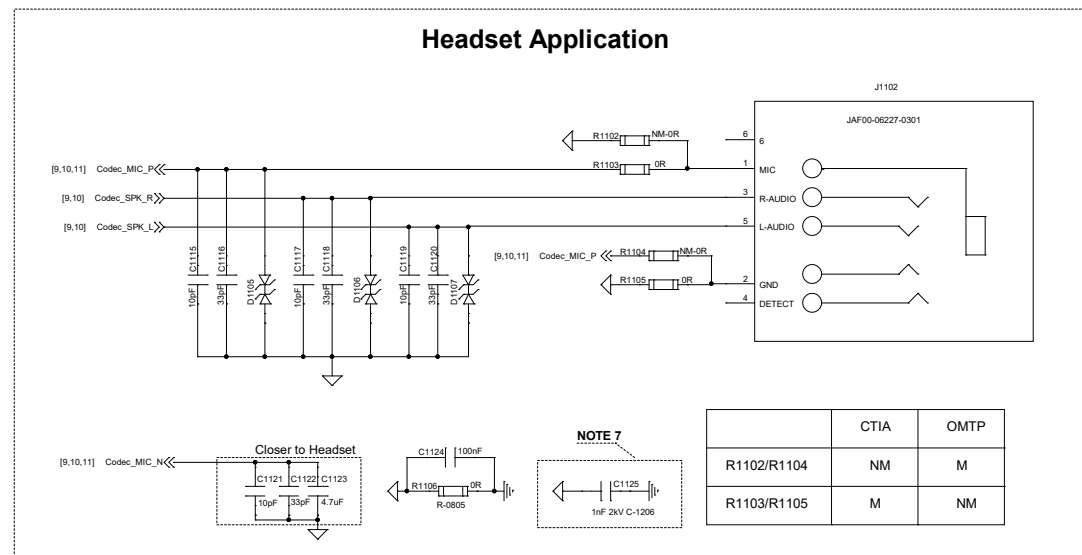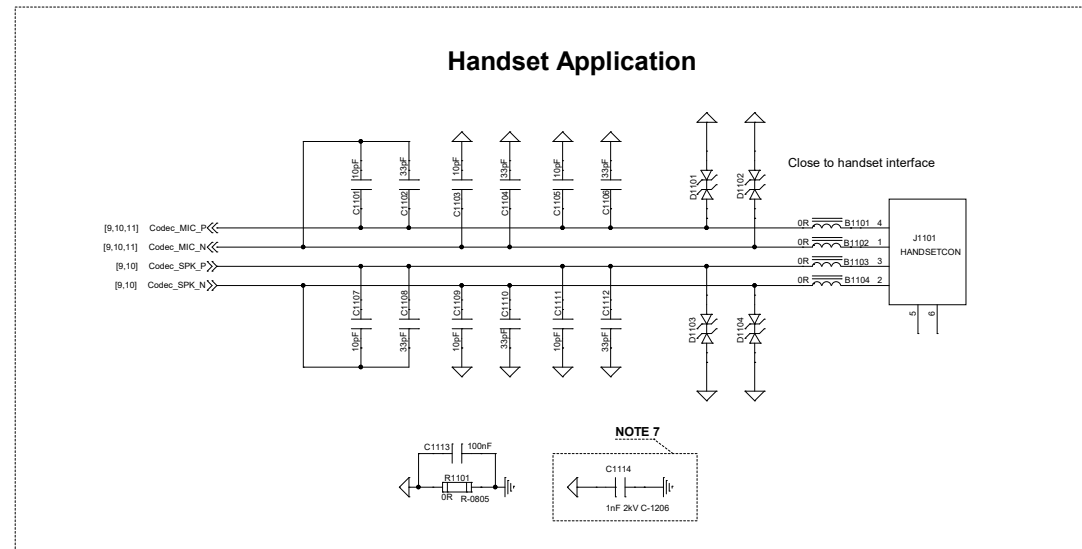


NOTE:

- The codec analog output can drive handset and headset. For larger power loads such as loudspeaker, an audio power amplifier should be added in the design.
- In handset application, both the MIC and SPK signal traces need to be routed as differential pairs.
- In headset application, the MIC signal traces need to be routed as a differential pair.
- All MIC and SPK signal traces should be surrounded with ground on the layer and ground planes above and below, and far away from noises such as clock and DC-DC signals, etc.
- Pay attention to the distinction between analog ground and digital ground. The analog ground and digital ground need to be connected with a 0Ω resistor packaged as R-0805 (a via directly to main GND).
- You can choose either ALC5616 or NAG88C10YG in audio codec design.
- C1114 and C1125 capacitors are used for ESD protection, they need to be placed close to D1101, D1102, D1103, D1104, D1105, D1106 and D1107 respectively, and connected to the main ground nearby.

Quectel Wireless Solutions

PROJECT	UC200A-GL	VER	1.0
DRAWN BY	Coco CHEN	CHECKED BY	Shiye ZHU
DATE	Friday, March 05, 2022	SIZE	A2
		SHEET	11 OF 13

SD Card Interface Design

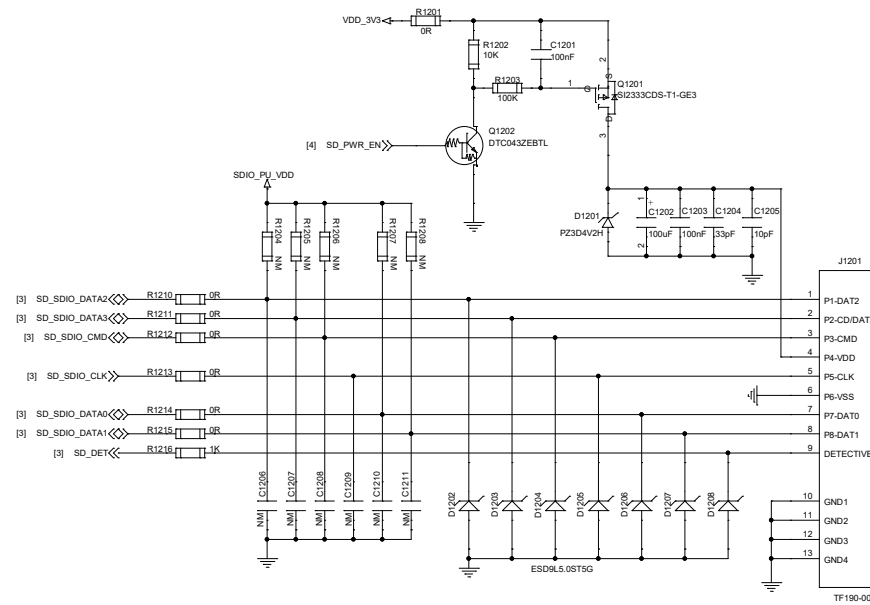

NOTE:


- The SDIO_PU_VDD can only be used for the pull-up resistor of SDIO bus and its maximum output current is 50 mA.
- The supply voltage range of VDD for SD card is 2.7–3.6 V and a sufficient current up to 0.8 A should be provided.
- To avoid the jitter of bus, pull-up resistors R1204–R1208 are recommended to be added to SDIO bus. SDIO_PU_VDD should be used as the pull-up power.
The value of these resistors are among 10–100 kΩ and the recommended value is 100 kΩ.
- In order to improve the signal quality, it is recommended to add 0 Ω resistors R1210–R1215 in series between the module and the SD card connector.
The bypass capacitors C1206–C1211 are reserved and not mounted by default.
- In order to offer good ESD protection, it is recommended to add electrostatic protective devices on SD card pins near the SD card connector with junction capacitance less than 15 pF.
- Keep SDIO signals far away from other sensitive circuits/signals such as RF circuits, analog signals, etc, as well as noisy signals such as clock and DC-DC signals, etc.
- It is important to route the SDIO signal traces with ground surrounded. The impedance of SDIO data trace is 50 Ω (±10 %).
- It is recommended to keep the traces of SD_SDIO_CLK, SD_SDIO_DATA[0:3] and SD_SDIO_CMD with equal length (the difference among them is less than 1 mm) and the total routing length needs to be less than 50 mm.
- Make sure the adjacent trace spacing is twice the trace width and the bus capacitance is less than 15 pF.

Quectel Wireless Solutions

PROJECT	UC200A-GL	VER	1.0
DRAWN BY	Coco CHEN	CHECKED BY	Shiye ZHU
DATE	Friday, March 08, 2022	SIZE	A2
		SHEET	12 OF 13

Other Designs


Indicators

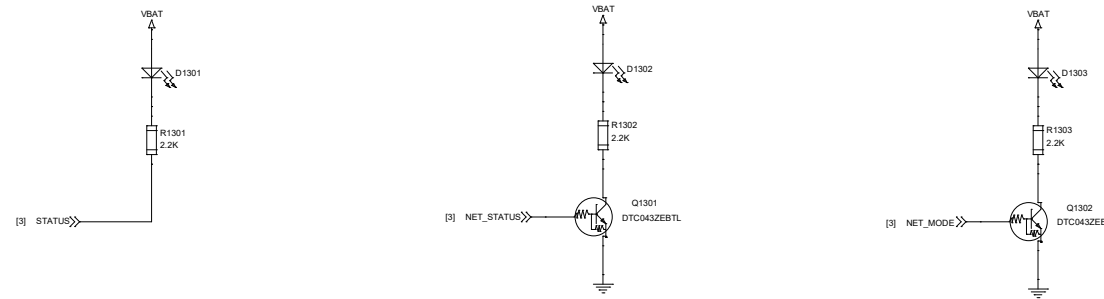

NOTE:

1. The STATUS is an open drain output pin.
2. For more details about STATUS, NET_STATUS and NET_MODE, see the hardware design document of the module.
3. If the low current consumption is required when your device is in sleep status, replace the power supply VBAT of the STATUS, NET_STATUS and NET_MODE indicators with the external controllable ones, which can be turned off when the module is in sleep mode to reduce the power consumption.


Reserved Test Points

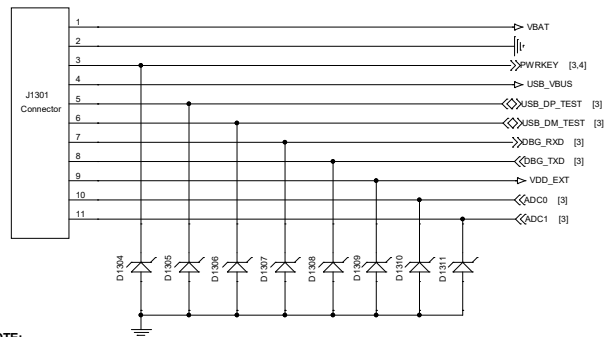

NOTE:

1. Test points for both USB and debug UART interfaces are reserved for capturing logs.
2. Test points for USB interface can also be reserved for firmware upgrading.
3. The junction capacitance of the ESD protection components on USB data lines should be less than 2 pF.
4. The debug UART interface supports 1.8 V power domain, and a level-shifting circuit should be used if the power domain of your application is 3.3 V.

USB_BOOT Interface

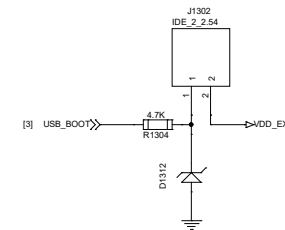

NOTE:

1. It is recommended to reserve the USB_BOOT interface design.
2. USB_BOOT is kept open by default. Pull USB_BOOT up to VDD_EXT before the module starts up, thus the module will enter emergency download mode when powered up. In this mode, the module supports firmware upgrading over USB interface.

Quectel Wireless Solutions

PROJECT	UC200A-GL	VER	1.0
DRAWN BY	Coco CHEN	CHECKED BY	Shiyou ZHANG
DATE	Friday, March 08, 2023	SHEET	13 OF 13